


Name: _____

Date: _____


Section C D F

Circuitry III

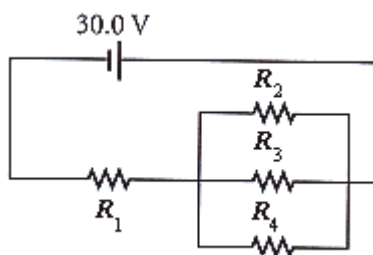1. An $11.0\ \Omega$ resistor and a $6.0\ \Omega$ resistor are connected in series with a battery. The potential difference across the $6.0\ \Omega$ resistor is measured as $9\ \text{V}$. Find the potential difference across the battery. (Your answer should be between $20 - 30\ \text{Volts}$)
2. A $18.0\ \Omega$ resistor and a $6.0\ \Omega$ resistor are connected in parallel to a battery, and the current in the $18.0\ \Omega$ resistor is found to be $0.45\ \text{A}$. Find the potential difference across the battery. (Your answer should be between $5 - 10\ \text{Volts}$)
3. Two identical parallel-wired strings of 40 bulbs are connected to each other in series. If the equivalent resistance of the combination is $130.0\ \Omega$ when it is connected across a potential difference of $120.0\ \text{V}$, what is the resistance of each individual bulb? (Your answer should be between $2 - 3\ \text{k}\Omega$)
4. Find the equivalent resistance of the circuit shown below, if $R_1 = 13.0\ \Omega$, $R_2 = 24.0\ \Omega$, $R_3 = 10.0\ \Omega$ and $R_4 = 3.0\ \Omega$. (Your answer should be between $15 - 20\ \Omega$)



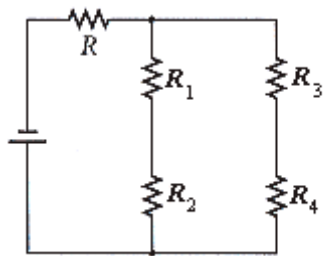5. The equivalent resistance of the circuit below is $60.0\ \Omega$. If $R_1 = 45.0\ \Omega$, $R_2 = 5.0\ \Omega$, $R_3 = 5.0\ \Omega$ and $R_4 = 45.0\ \Omega$, find the resistance of R . (Your answer should be between $34 - 40\ \Omega$)



6. Re-draw the schematic diagram below, and then find the equivalent resistance of the circuit. Let $R_1 = 8.0\ \Omega$, $R_2 = 6.0\ \Omega$, $R_3 = 7.0\ \Omega$, $R_4 = 6.0\ \Omega$ and $R_5 = 4.5\ \Omega$. (Your answer should be between $15 - 20\ \Omega$)

