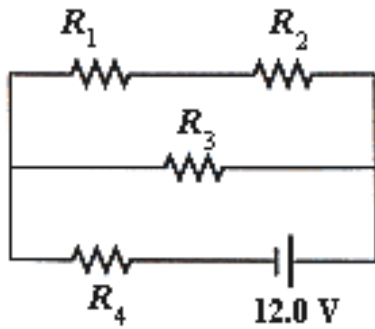


- Two resistors, A and B , are connected in series to a 6.0 V battery. A voltmeter connected across resistor A measures a potential difference of 2.4 V . When the two resistors are connected in parallel across the 6.0 V battery, the current in B is found to be 1.2 A . Find the resistances of A and B . (Your should find that $A \neq B$, but both resistances should be less than $10\ \Omega$)
- Three resistors are connected in parallel – an $80\ \Omega$ resistor, a $16.0\ \Omega$ resistor, and a $20\ \Omega$ resistor, and then joined in series to a $12.0\ \Omega$ resistor from a battery source with a potential difference of 24.0 V .
 - Draw a schematic diagram for this circuit.
 - Calculate the equivalent resistance and the net current in the circuit. (Your answers should be between $15 - 22\ \Omega$, and $1 - 2\text{ A}$, respectively)
 - Find the current and potential difference in each resistor. (Remember your rules)

3. Four resistors are connected to a battery with a terminal voltage of 12.0 V, as shown in the figure below. Assume that $R_1 = 30.0\ \Omega$, $R_2 = 80.0\ \Omega$, $R_3 = 100.0\ \Omega$ and $R_4 = 15.0\ \Omega$)



- a. Re-draw the circuit.

- b. Determine the equivalent resistance and the net current in the circuit. (Your answer should be between $50 - 70\ \Omega$, and $0 - 1\ \text{A}$, respectively.)
- c. Determine the potential difference in the $30\ \Omega$ resistor. (Your answer should be between $2 - 3\ \text{V}$)