

Name _____

Date _____

Circuitry Drawings



**ISTANBUL
INTERNATIONAL
COMMUNITY
SCHOOL**

1. In the circuit below, which meter is **not** correctly connected?

