

Name _____

Date _____



Circuitry I

1. A net charge of 51 mC passes through the cross-sectional area of a wire in 14.0 s.
 - A. What is the current in the wire? Give your answer in mA.

 - B. How many electrons pass the cross-sectional area in 1.0 min? (Your answer should be between 1×10^{15} and 1×10^{20} electrons)

2. How much charge passes through a cross-sectional area of a copper wire in 1.0 s if $I = 6.5$ A?

3. The element of an electric heater has a resistance R when in operation. What is the resistance of a second heater that has a power output three times as large at the same operating voltage?
 - A. $\frac{R}{9}$
 - B. $\frac{R}{3}$
 - C. $3R$
 - D. $9R$

4. In the diagram, the voltmeter V has a resistance of $100\text{ k}\Omega$ and is connected such as to measure the potential difference across the $100\text{ k}\Omega$ resistor. The battery has an emf of 5.0 V and negligible internal resistance.